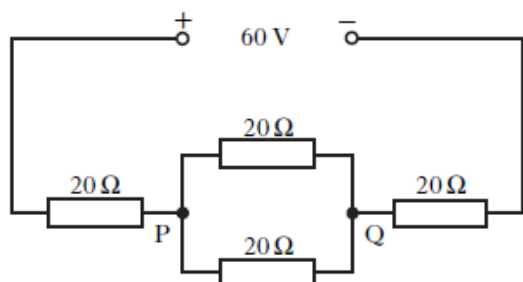


Unit 3 – Electricity

Section 2 – Current, Potential Difference, Power & Resistance


- 2007** 9. Four resistors, each of resistance $20\ \Omega$, are connected to a $60\ \text{V}$ supply of negligible internal resistance, as shown.



The potential difference across PQ is

- A $12\ \text{V}$
- B $15\ \text{V}$
- C $20\ \text{V}$
- D $24\ \text{V}$
- E $30\ \text{V}$

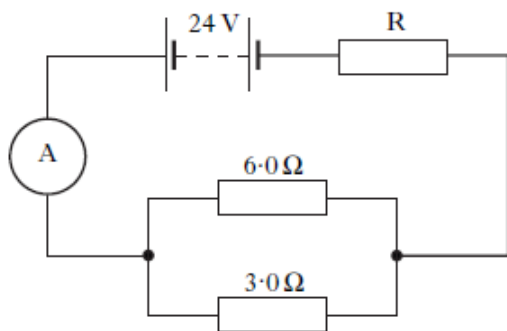- 2009** 9. A battery of e.m.f. $24\ \text{V}$ and negligible internal resistance is connected as shown.








The reading on the ammeter is $2.0\ \text{A}$.

The resistance of R is

- A $3.0\ \Omega$
- B $4.0\ \Omega$
- C $10\ \Omega$
- D $12\ \Omega$
- E $18\ \Omega$

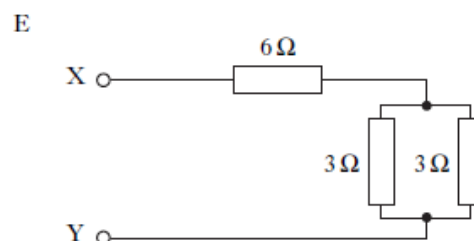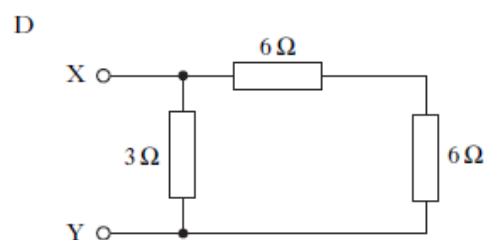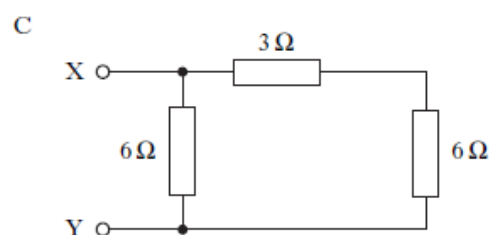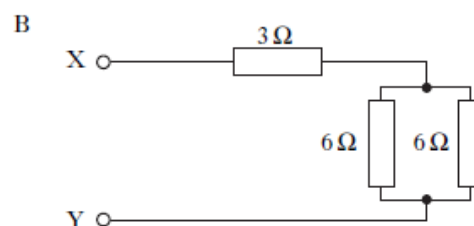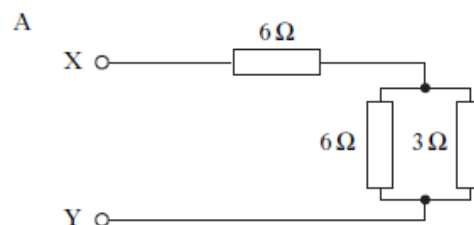
- 2010** 9. Which of the following combinations of resistors has the greatest resistance between X and Y?



2011 8. One volt is equivalent to one

- A farad per coulomb
- B ampere per ohm
- C joule per ampere
- D joule per ohm
- E joule per coulomb.

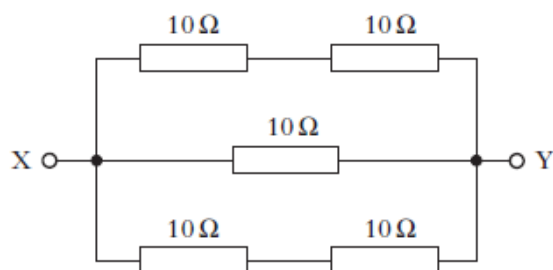
2012 9. The diagram shows part of an electrical circuit.



What is the resistance between X and Y?

- A 0.2 Ω
- B 5 Ω
- C 10 Ω
- D 20 Ω
- E 50 Ω

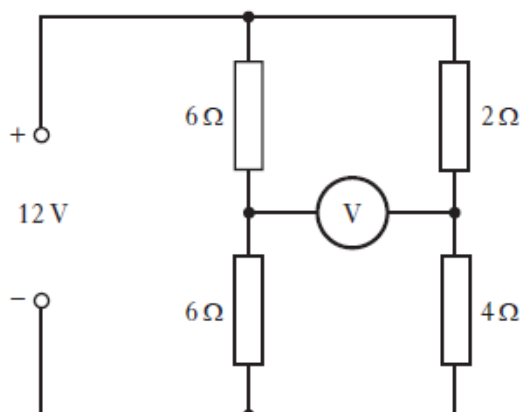
2013 Revised 17. The following circuit is set up.



The reading on the voltmeter is

- A 0 V
- B 2 V
- C 6 V
- D 8 V
- E 12 V.

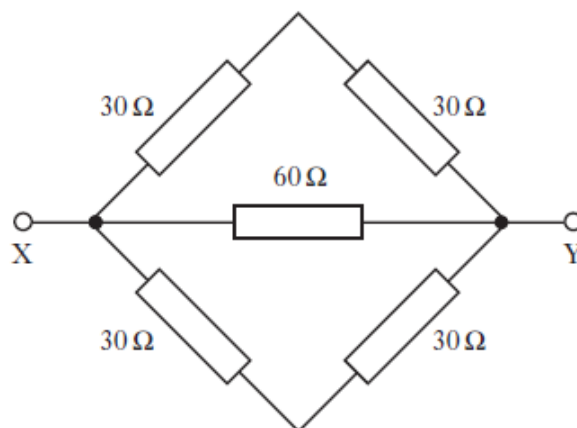
2014 8. Five resistors are connected as shown.



The resistance between X and Y is

- A 12 Ω
- B 20 Ω
- C 30 Ω
- D 60 Ω
- E 180 Ω.

2014 9. A circuit is set up as shown.

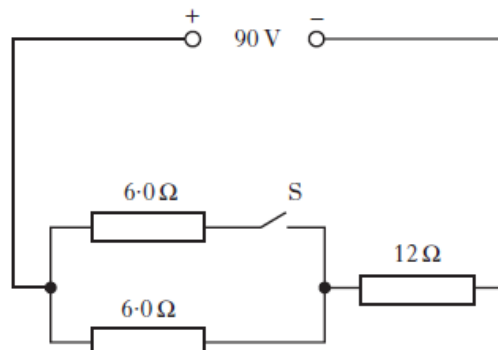


The internal resistance of the supply is negligible.

Which row in the table shows the potential difference (p.d.) across the 12 Ω resistor when switch S is open and when S is closed?

	<i>p.d. across 12 Ω resistor when S is open/V</i>	<i>p.d. across 12 Ω resistor when S is closed/V</i>
A	30	18
B	45	45
C	60	45
D	60	72
E	72	60

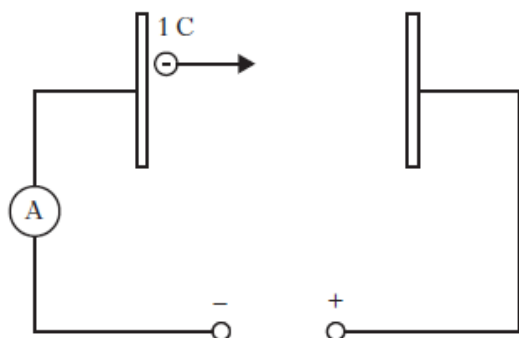
- 2015** 8. One joule of work is done in moving one coulomb of charge between two plates as shown.



From the information given, which of the following statements must be true?

- A The distance between the plates is one metre.
- B The capacitance of the circuit is one farad.
- C The current in the circuit is one ampere.
- D The potential difference between the plates is one volt.
- E The resistance of the circuit is one ohm.

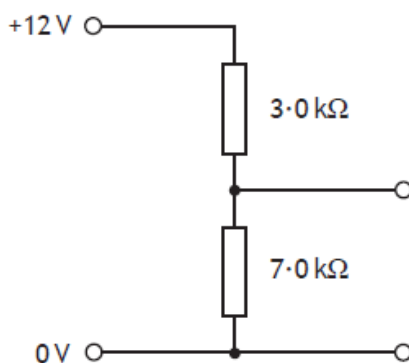
- 2016** 18. A potential divider circuit is set up as shown.



The potential difference across the $7.0 \text{ k}\Omega$ resistor is

- A 3.6 V
- B 4.0 V
- C 5.1 V
- D 8.4 V
- E 9.0 V

2018 15. A circuit is set up as shown.

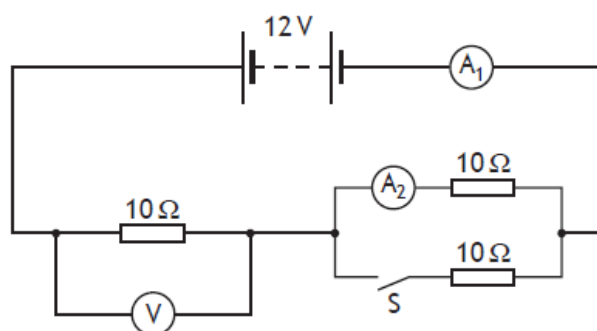

The battery has negligible internal resistance.

A student makes the following statements about the readings on the meters in this circuit.

- I When switch S is open the reading on the voltmeter will be 6.0 V .
- II When switch S is open the reading on A_2 will be 0.60 A .
- III When switch S is closed the reading on A_1 will be 0.80 A .

Which of these statements is/are correct?


- A I only
- B II only
- C I and II only
- D II and III only
- E I, II and III

2018 16. The power dissipated in a $120\ \Omega$ resistor is 4.8 W .

The current in the resistor is

- A 0.020 A
- B 0.040 A
- C 0.20 A
- D 5.0 A
- E 25 A .

2019 23. A circuit is set up as shown.

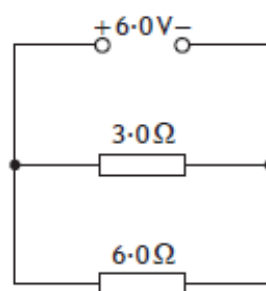


The power supply has negligible internal resistance.

The power dissipated in the $3.0\ \Omega$ resistor is

- A $3.0\ \text{W}$
- B $6.0\ \text{W}$
- C $9.0\ \text{W}$
- D $12\ \text{W}$
- E $18\ \text{W}$.

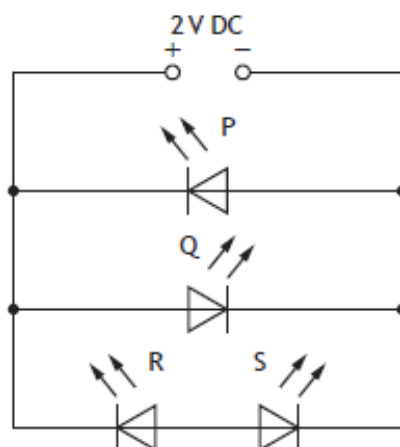2019 24. A student connects four identical light emitting diodes (LEDs) to a 2 V DC supply as shown.



Which of the LEDs P, Q, R, and S will light?

- A P only
- B Q only
- C P and Q only
- D P and R only
- E Q and S only.